

MATURITY

ACL406AS - Direct AC Line LED Driver UP TO 6W OUTPUT ACL406AS-AC 450 to 650 lumen-AN-V1.3 – JUNE 2021

Application Notes



1. FEATURES

ACL406AS up to 6W output,

- Direct AC Line LED Driver requiring few external components,
- Wide AC Input Range: 50 to 280V AC,
- High Power Factor: > 0.98 with optimized LED configuration,
- Low harmonic content: THD < 15% (typ.),
- Low quiescent current: 120μA,
- High Efficiency: 85% typical,
- Ultra-Flexible LED Forward Voltage Configuration,
- Up to 4 LED stages capability,
- Low Flicker: according to applications (need to external components: see application note for more information),
- Percentage flicker: 25%,
- Flicker index: 10%,
- Over Temperature Power derating

2. APPLICATIONS

- General Solid-State Lighting,
- Medium Power LED Lamp,
- Connected Medium Power Led Lamp,
- Industrial High power LED Lamp.

3. DESCRIPTION

The ACL406AS is an AC direct LED driver requiring few external components: a diode bridge to rectify the AC voltage and a resistor to tune the LED current.

Multiple ACL406AS AC line drivers can be used in parallel to drive high power LED systems for industrial applications.

4. PIN CONNECTIONS

١

	r	
NC 💷	EP	D2
GND 💷	GND	💷 D3
RSET 💷	i	D4

Figure 1: SO8 with Exposed Pad (TOP VIEW)



5. TYPICAL APPLICATION: HIGH RELIABILITY AC 230VAC ENTRY-LEVEL LAMP (RECOMMENDED)



Figure 2: Recommended Low-cost application schematic for 230V_{AC}

Options:

- RSET = 31.6 Ω , the light is at 524 lumens with 6 LED (LED at 120 lm/W). In this design, only 7 components + 6 LEDs on the PCB. ⊳
- ≻ RSET = 20 Ω , the light is at 727 lumens with 12 LED (LED at 120 lm/W). In this design, only 7 components + 12 LEDs on the PCB.

Rset	P sector	PLED	PLUM	PF	Efficiency	Percentage flicker (%)	Flicker index (%)
31.6 Ω	4.98 W	4.37 W	524 lm	0.98	87.8 %	100 %	33.9 %
20 Ω	6.87 W	6.05 W	727 lm	0.98	88.1 %	100 %	33.9 %
20 Ω	6.87 W	6.05 W	727 lm	0.98	88.1 %	100 %	33.

Table 1: Characteristics of the bulb

Calculations of ILED @25°C for each stage are:

- I_{D1}=0.88/(10+R_{SET}) in A, \triangleright
- ≻ ID2=0.93/(10+RSET) in A,
- $I_{D3}=1.02/(10+R_{SET})$ in A, ⊳
- ID4=1.20/(10+RSET) in A.
- ≻

The LED current is summarized below:

RSET	Conditions	I _{D1}	I _{D2}	I _{D3}	I _{D4}
31.6 Ω	@25°C	21.2 mA	22.4 mA	24.5 mA	28.8 mA
20 Ω	@25°C	29.3 mA	31.0 mA	34.0 mA	40.0 mA

Table 2: LED currents

вом:

Item	QTY	Designator	Description
1	1	C1	Capacitor 1210 450V 0.1uF X7T 20%
2	1	D1	Bridge Rectifier 500mA 600V SMD TO-269AA
3	1	D2	DIODE TVS 376V 602V DO214AA
4	6 or12	LED1 to LED6, and / or LED11 to LED16	LED 48V, 20mA, 4000K, BIN=5, 120lm, code 40M, case 2835
5	2	R1, R3	Resistor, Thin Film, 62R, 5%, 0.25W, 1206
c	1	20	RES SMD 20 OHM 5% 1/4W 0603 (case with 12 LED)
D	T	RZ	RES SMD 31.6 OHM 1% 1/4W 0603 (case with 6 LED)
7	1	RV1	VARISTOR 430V 250A 2SMD
8	1	U1	Direct AC line LED driver Full range

Table 3: BOM for reference only



6. TYPICAL APPLICATION: LOW-COST AC 230VAC LIGHT WITHOUT ELECTRIC PROTECTION





Figure 3: Not Recommended - Low-cost application schematic for 230V_{AC}

In this design, the light is like the recommended schematic but without electric protections! Only the fuse resistor is placed before the bridge rectifier. In this case, it's only 4 components on the PCB to have 500 lumen lights (or 10 components with LED).

Options:

- RSET = 31.6 Ω, the light is at 524 lumens with 6 LED (LED at 120 lm/W). In this design, only 4 components + 6 LEDs on the PCB.
- RSET = 20 Ω, the light is at 727 lumens with 12 LED (LED at 120 lm/W). In this design, only 4 components + 12 LEDs on the PCB.

R _{SET}	P sector	PLED	PLUM	PF	Efficiency	Percentage flicker (%)	Flicker index (%)
31.6 Ω	4.98 W	4.37 W	524 lm	0.98	87.8 %	100 %	33.9 %
20 Ω	6.87 W	6.05 W	727 lm	0.98	88.1 %	100 %	33.9 %

BOM:

QTY	Designator	Description
1	D1	Bridge Rectifier 500mA 600V SMD TO-269AA
6 or12	LED1 to LED6, and / or LED11 to LED16	LED 48V, 20mA, 4000K, BIN=5, 120lm, code 40M, case 2835
1	R1	Resistor, Thin Film, 3R9, 5%, 0.25W, 1206
1 1 02		RES SMD 20 OHM 5% 1/4W 0603
4 1	κz	RES SMD 31.6 OHM 1% 1/4W 0603
1	U1	Direct AC line LED driver Full range
	QTY 1 6 or12 1 1 1	QTY Designator 1 D1 6 or12 LED1 to LED6, and / or LED11 to LED16 1 R1 1 R2 1 U1

Table 4: BOM for reference only



Example of PCBA:



Figure 4: PCBA with ACL406AS at 230V_{AC}. IMS PCB, diameter 40 mm, thickness 1.6 mm.

IMPORTANT NOTICE AND DISCLAIMER

EASII IC PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD-PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with EASii IC products. You are solely responsible for (1) selecting the appropriate EASii IC products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. EASii IC grants you permission to use these resources only for development of an application that uses the EASii IC products described in the resource. Other reproduction and display of these resources are prohibited. No license is granted to any other EASii IC intellectual property right or to any third-party intellectual property right. EASii IC disclaims responsibility for, and you will fully indemnify EASii IC and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources. EASii IC's products are provided subject to EASii IC's Terms of Sale (www.easii-ic.com/en/legal/termsofsale.php) or other applicable terms available either on easii-ic.com or provided in conjunction with such EASii IC products. EASii IC's provision of these resources does not expand or otherwise alter EASii IC's applicable warranties or warranty disclaimers for EASii IC products.



EASii IC France: 90, Avenue Leon Blum 38100 Grenoble – France Copyright © 2019 EASii IC Sales-IC@easii-ic.com http://www.easii-ic.com